

HW 1

① $g_{m0} = \frac{250\mu S}{1V_{GS}}$ $g_{m0} = \frac{250\mu S}{4}$
 $g_{m0} = 6.25 \mu S$

$g_m = \frac{0.0081 - 0.005}{-0.5 - 1.5} = 3.1 \mu S$

5) $g_m = g_{m0} \left(\frac{1 - V_{GS}}{V_{GS}} \right)$
 $= \left(\frac{250\mu S}{1V} \right) \left(\frac{1 - V_{GS}}{V_{GS}} \right)$
 $6 \times 10^{-3} = \frac{250\mu S}{2.5} \left(1 - \frac{1}{2.5} \right)$
 $I_{DSS} = 12.5 \text{ mA}$

e) $g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS0}} \right)$
 $= 0.004 \left(1 - \frac{1}{5} \right)$
 $= 3.2 \mu S$

9) $Z_o = \frac{1}{g_m} = \frac{1}{25 \times 10^{-6}} = 40 \text{ k}\Omega$
 $Z_o = r_d = 40 \text{ k}\Omega$
 $A_v (FET) = -g_m r_d$
 $= -(4.5 \times 10^{-3}) (40 \times 10^3)$
 $A_v (FET) = -180$

13a) $g_m = 75 \mu S$
 $g_m = 75 \mu S$
 $= 0.75 \text{ ms}$

b) $r_d = \frac{1}{g_m}$
 $= \frac{1}{10 \times 10^{-6}}$
 $r_d = 100 \text{ k}\Omega$

11a) $g_{m0} = \frac{250\mu S}{1V_{GS}}$ $g_{m0} = \left(\frac{250 \times 0.010}{5} \right)$
 $= 4 \mu S$

7) $Z_i = R_G, Z_o = R_D$
 $Z_o = R_D || r_d$
 $= (11.8 \times 10^3) || (40 \times 10^3)$
 $Z_o = 1.722 \text{ k}\Omega$

b) $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$
 $g_m = \frac{0.010 - 0.0064}{0 - (-1)}$
 $= 3.6 \mu S$

$A_v = -g_m (R_D || r_d)$
 $g_m = \frac{250 \times 0.010}{6} \left(1 - \frac{1.5}{-6} \right) = 2.5 \mu S$
 $A_v = (-0.0025) (1722) = -4.305$

c) $g_m = g_{m0} \left(\frac{1 - V_{GS}}{V_{GS}} \right)$
 $g_m = 0.004 \left(1 - \frac{0.05}{-5} \right)$
 $= 3.6 \mu S$

21) $Z_i = 10 \text{ M}\Omega$
 $Z_o = \frac{4 + (5 \times 1.1) + (1.1/20)(3.3 \times 10^3)}{1 + (3 \times 1.1) + \frac{3.3 + 1.1}{20}}$
 $Z_o = 3179.15 \Omega$
 $A_v = \frac{4(3)(2.2)}{1 + (3)(1.1) + \frac{3.3 + 1.1}{20}} = -2.19$

d) $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$

$$23) a) V_{ES} = -5.366V$$

$$R_s = \frac{V_{ES}}{-I_D} = \frac{-5.366}{-0.976 \times 10^{-3}}$$

$$= 5.498 k\Omega$$

$$b) I_D = 1.155 mA$$

$$V_{GS} = -5.13V$$

$$R_s = \frac{V_{GS}}{-I_D} = \frac{-5.13}{-1.155 \times 10^{-3}}$$

$$= 4.43 k\Omega$$

$$25) Z_i = R_1 \parallel R_2 \quad Z_o = r_d \parallel R_o$$

$$Z_i = 11 \parallel 82 \quad Z_o = 50 \parallel 2$$

$$Z_i = 9.7 m\Omega \quad Z_o = 1.92 k\Omega$$

$$A_v = -g_m Z_o$$

$$A_v = -g = (5.47 \times 10^{-3})(1.92 \times 10^3)$$

$$= -10.5 \Rightarrow Z_o = 1.96 k\Omega$$

$$V_o = A_v V_i$$

$$= (-10.5)(20 \times 10^{-3}) = -210 mV$$

$$V_o = -210 mV \Rightarrow P_o = 214.4 \mu W$$

$$27) Z_i = A_v \parallel R_n$$

$$Z_i = 11 \parallel 82$$

$$Z_i = 9.7 M\Omega$$

$$Z_o = r_d \parallel R_o$$

$$Z_o = 20 \parallel 2 = 1.82 k\Omega$$

$$V_o = (-9.94)(20 \times 10^3) = -198.8 mV$$

$$29) Z_i = R_s \parallel \frac{1}{g_m} \Rightarrow Z_i = 1500 \parallel \frac{1}{2.14 \times 10^{-3}}$$

$$= 356.3 \Omega$$

$$Z_o = R_o = 33 k\Omega$$

$$V_o = (7.06)(4 \times 10^{-3}) = 28.24 mV$$

$$31) Z_i = R_s \parallel \frac{1}{g_m}$$

$$Z_i = 100 \parallel \frac{1}{2.63 \times 10^{-3}} = 275.5 \Omega$$

$$Z_o = 2.2 k\Omega \quad Z_o = R_p$$

$$A_v = g_m R_p$$

$$= (2.63 \times 10^{-3})(2200) = 5.79$$

$$32) Z_i = A_v \parallel R_{L_i} \quad Z_i = 10 M\Omega$$

$$Z_o = R_s \parallel \frac{1}{g_m}$$

$$Z_o = (2.2 \times 10^3) \parallel \frac{10^3}{1.511}$$

$$= 508.7 \Omega$$

$$A_v = \frac{g_m R_L}{1 + g_m R_s} = \frac{(1.511)(2.2)}{1 + (1.511)(2.2)}$$

$$= 0.77$$

$$36) Z_i = 10 M\Omega$$

$$Z_o = r_d \parallel R_o = 1.8 k\Omega$$

$$A_v = -g_m R_o = -(5.4)(1.8) = -9.72$$

$$39) Z_i = 10 \parallel 91 \quad Z_i = 9 M\Omega$$

$$Z_o = 45 \parallel 11 \parallel \frac{1}{4.13} = 197.6 \Omega$$

$$A_v = \frac{1 + (4.13)(1.074)}{R_f + r_d \parallel R_o} = 0.816$$

$$41) Z_i = \frac{R_f + r_d \parallel R_o}{1 + g_m(R_f + r_d \parallel R_o)}$$

$$= R_i = 1.73 M\Omega$$

$$Z_o = 10000 \parallel 100 \parallel 2.2 = 2.15 k\Omega$$

$$A_v = -g_m (R_f \parallel r_d \parallel R_o)$$

$$= -(2.22)(2.15) = -4.77$$

$$45) V_o = V_i A_v \Rightarrow V_o = (0.8)(-4.097)$$

$$= -3.28 mV$$

$$A_v = -g_m (r_d || R_D)$$

$$A_v = -(1.344)(40113.2) = -4.097$$

$$47) R_s = \frac{-V_{gsa}}{I_{DQ}} = \frac{-1}{5.33 \times 10^{-3}}$$

$$= \underline{187.62 \Omega}$$

$$40 R_D = 1.876 R_D + 75.04$$

$$R_D = \underline{1.97 k\Omega}$$

$$R_D \approx \underline{2 k\Omega}$$