

Electronics Test 2

$$1. V_o = \left(1 + \frac{R_F}{R_i}\right) V_i = \left(1 + \frac{750 \times 10^3}{30 \times 10^3}\right) (150 \text{ mV}_{\text{rms}}) = (21.8333)(150 \times 10^{-3}) \text{ V}_{\text{rms}}$$

$$V_o = 3.275 \text{ V}_{\text{rms}}$$

Hence, the output voltage of the op-amp amplifier, V_o is $3.275 \text{ V}_{\text{rms}}$

$$2. V_{o1} = -\frac{R_F}{R_i} (V_i) = -\frac{330 \text{ k}\Omega}{33 \text{ k}\Omega} (12 \text{ mV}) = -(10)(12 \times 10^{-3})$$

$$V_{o1} = -120 \text{ mV}$$

$$V_o = -\left[\left(\frac{R_{f2}}{R_2}\right) V_{o1} + \left(\frac{R_{f2}}{R_3}\right) V_2\right] = -\left[\left(\frac{470 \text{ k}\Omega}{47 \text{ k}\Omega}\right) (-120 \text{ mV}) + \left(\frac{470 \text{ k}\Omega}{47 \text{ k}\Omega}\right) (18 \text{ mV})\right]$$

$$= -\left[(10)(-120 \times 10^{-3}) + (10)(18 \times 10^{-3})\right] = -[-1.2 + 0.18]$$

$$V_o = 1.02 \text{ V}$$

Hence, the output voltage of summing amplifier is 1.02 V

$$3. f_{oL} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi (10 \text{ k}\Omega)(0.05 \mu\text{F})} = \frac{1}{2\pi (10 \times 10^3)(0.05 \times 10^{-6})}$$

$$f_{oL} = 318.3 \text{ Hz}$$

Hence, the lower cutoff frequency of the bandpass filter is 318.3 Hz

$$f_{oH} = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi (20 \text{ k}\Omega)(0.02 \mu\text{F})} = \frac{1}{2\pi (20 \times 10^3)(0.02 \times 10^{-6})}$$

$$f_{oH} = 397.89 \text{ Hz}$$

Hence, the upper cutoff frequency of the bandpass filter is 397.9 Hz

$$4. (a) I_{dc} = \frac{2}{\pi} I_p = \frac{2}{\pi} \left(\frac{20 \text{ V}}{4 \Omega}\right) = \frac{40}{12.57} = 3.18$$

$$I_{dc} = 3.18 \text{ A}$$

$$P_i = (3.18 \text{ A})(22 \text{ V})$$

$$P_i = 70 \text{ W}$$

$$P_o = \frac{(20 \text{ V})^2}{2(4 \Omega)} = \frac{400}{8}$$

$$P_o = 50 \text{ W}$$

$$\% \eta = \frac{50\text{W}}{70\text{W}} \times 100\%$$

$$\% \eta = 71.43\%$$

Therefore, the efficiency for the amplifier is 71.43%

$$(b) I_{dc} = \frac{2}{\pi} I_p = \frac{2}{\pi} \left(\frac{4\text{V}}{4\Omega} \right) = \frac{8}{12.57} = 0.637$$

$$I_{dc} = 0.637\text{A}$$

$$P_i = (0.637\text{A})(28\text{V})$$

$$P_i = 17.8\text{W}$$

$$P_o = \frac{(4\text{V})^2}{2(4\Omega)} = 4$$

$$P_o = 4\text{W}$$

$$\% \eta = \frac{P_o}{P_i} \times 100\% = \frac{4\text{W}}{17.8\text{W}} \times 100\%$$

$$\% \eta = 22.47\%$$

Therefore, the efficiency for the amplifier is 22.47%

$$5. (a) I_{dc} = \frac{2}{\pi} I_p = \frac{2}{\pi} \left(\frac{8\sqrt{2}}{8\Omega} \right) = \frac{2.828}{3.14} = 0.900$$

$$I_{dc} = 0.9\text{A}$$

$$P_i = (0.9\text{A})(30\text{V})$$

$$P_i = 27\text{W}$$

Hence, the input power dissipation of amplifier is 27W

$$(b) P_o = \frac{V_L^2}{R_L} = \frac{(8\text{V})^2}{8\Omega} = 8$$

$$P_o = 8\text{W}$$

Hence, the output power dissipation of amplifier is 8W

$$6. \text{Resolution} = \frac{V_{REF}}{2^n} = \frac{10\text{V}}{2^{14}} = \frac{10}{4096}$$

$$\text{Resolution} = 2.44\text{mV/count}$$

Hence, the resolution of the ladder network is 2.44mV/count

$$7. f_0 = \frac{0.3}{R_1 C_1} = \frac{0.3}{(4.7 \text{ k}\Omega)(0.001 \mu\text{F})} = \frac{0.3}{4.7 \times 10^{-6}}$$

$$f_0 = 63.8 \text{ KHz}$$

$$f_1 = \pm 8f_0 = \pm 8(63.8 \text{ KHz})$$

V 6V

$$f_1 = 85.1 \text{ KHz}$$

Hence, the lock range of the PLL circuit is 85.1 KHz