

Ahmed EL QAOUA

Test 2: Electronics 2:

$$\textcircled{1} V_o = \left(1 + \frac{R_F}{R_i}\right) V_1$$

$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_1$$

$$V_o = \left(1 + \frac{770 \times 10^3}{36 \times 10^3}\right) (150 \text{ mV}_{\text{rms}})$$

$$= (21.833) (150 \times 10^{-3}) V_{\text{rms}} = 40$$

$$\boxed{32.75 V_{\text{rms}}}$$

$$\textcircled{2} V^+ = V^- = 0$$

Apply KCL at node V^- in op Amp $\textcircled{1}$

$$\frac{0 - 12 \text{ mV}}{33 \text{ k}} + \frac{0 - V_{o1}}{330 \text{ k}} = 0$$

$$\boxed{V_{o1} = -0.12 \text{ V}}$$

Apply KCL at node V^- in op Amp $\textcircled{2}$

$$\frac{0 + 0.12}{47 \text{ k}} + \frac{0 - 18 \text{ mV}}{47 \text{ k}} + \frac{0 - V_o}{47 \text{ k}} = 0$$

$$\frac{V_o}{47 \text{ k}} + \frac{0.102}{47 \text{ k}} = 0 \Rightarrow \boxed{V_o = 1.02 \text{ V}}$$

③ Lower cut-off

$$f_{oL} = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi \times 10 \times 0.05 \times 10^{-6} \times 10^3}$$

$$f_{oL} = 318.3098 \text{ Hz}$$

Upper cut-off frequency

$$f_{oH} = \frac{1}{2\pi R_2 C_2} \Rightarrow f_{oH} = \frac{1}{2\pi \times 20 \times 10^3 \times 0.02 \times 10^{-6}}$$

$$f_{oH} = \frac{1}{2\pi \times 20 \times 0.02 \times 10^{-3}} \Rightarrow f_{oH} = 397.8873 \text{ Hz}$$

④ (a) $I_{dc} = \frac{2}{\pi} I_p$

$$I_{dc} = \frac{2}{\pi} \left(\frac{V_L}{R_L} \right)$$

$$I_{dc} = \frac{2}{\pi} \left(\frac{20}{12.57} \right) = \frac{40}{12.57} = 3.18 = \boxed{3.18 \text{ A}}$$

$$P_i = I_{dc} V_{cc}$$

$$\Rightarrow P_i = (3.18 \text{ A})(22 \text{ V}) = 70 \text{ W}$$

$$P_o = \frac{V_L^2}{2R_L} \Rightarrow P_o = \frac{(20 \text{ V})^2}{2(4 \Omega)} = \frac{400}{8} = \boxed{50 \text{ W}}$$

$$\% \eta = \frac{P_o}{P_i} \times 100\%$$

$$\% \eta = \frac{50W}{70W} \times 100\% = \boxed{71.43\%}$$

$$(b) I_{dc} = \frac{2}{\pi} I_p = \frac{2}{\pi} \left(\frac{V_L}{R_L} \right) = \frac{2}{\pi} \left(\frac{4V}{4\Omega} \right)$$

$$= \frac{8}{12.57} = \boxed{0.637}$$

$$P_i = I_{dc} V_{cc}$$

$$P_i = (0.637A)(22V) = 14W$$

$$P_o = \frac{V_L^2}{2R_L} \rightarrow P_o = \frac{(4V)^2}{2(4\Omega)} = \frac{4}{2} = 2W.$$

$$\% \eta = \frac{P_o}{P_i} \times 100\%$$

$$\% \eta = \frac{2W}{14W} \times 100\% = \boxed{14.3\%}$$

$$(5) (a) I_{dc} = \frac{2}{\pi} I_p$$

$$= \frac{2}{\pi} \left(\frac{V_o}{R_L} \right) = \frac{2}{\pi} \left(\frac{V_L \sqrt{2}}{R_L} \right)$$

$$I_{dc} = \frac{2}{\pi} \left(\frac{8V \sqrt{2}}{8\Omega} \right) = \frac{2.828}{8\Omega} = 0.9 = \boxed{0.9A}$$

$$P_i = I_{dc} V_{cc} = V$$

$$P_i = (0.9A)(30V) = \boxed{27W}$$

$$(b) P_o = \frac{V_L^2}{R_L} \Rightarrow P_o = \frac{(8V)^2}{8\Omega} = \frac{P}{1} = \boxed{8W}$$

$$(6) \text{ voltage resolution} = V_{ref} / 2^n \quad n=12$$

$$\Rightarrow V_{\text{resolution}} = 10 / 2^{12} = \frac{10}{4096} = \boxed{2.44 \times 10^{-3} V}$$

(7) Lock range of PLL circuit.

$$R_1 = 4.7k\Omega \quad \text{and} \quad C_1 = 0.01\mu F$$

$$f_{lock} = 1 \pm \frac{\beta f_{\phi}}{V}$$

$$\text{from (a)} \quad f_{\phi} = 631.82 \text{ Hz}$$

$$f_0 = \frac{0.3}{R_1 C_1} = \frac{0.3}{(4.7 \times 10^3)(0.001 \times 10^{-6})}$$

$$= \frac{0.3}{4.7 \times 0.001 \times 10^{-3}} = 6.38 \times 10^4$$

with limitation $2k\Omega \leq R_1 \leq 20k\Omega$, the lock range:

$$f_L = \pm \frac{8f_0}{V} = \pm \frac{8(6.38 \times 10^4)}{8} = \boxed{85 \text{ kHz}} \quad \text{Hz}$$