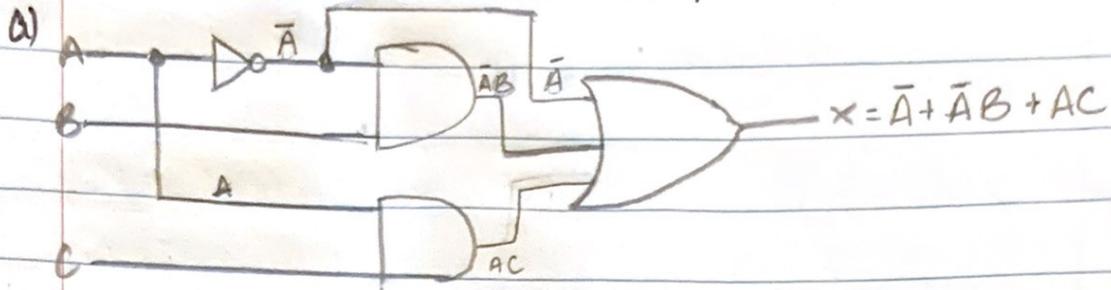


Isabella Symonette
 Digital Circuits Lab 3


Sept. 17, 2020

2. Write the output expression for each circuit.



A \ BC	00	01	11	10
0	1	1	1	1
1		1	1	

$X = \bar{A} + C$

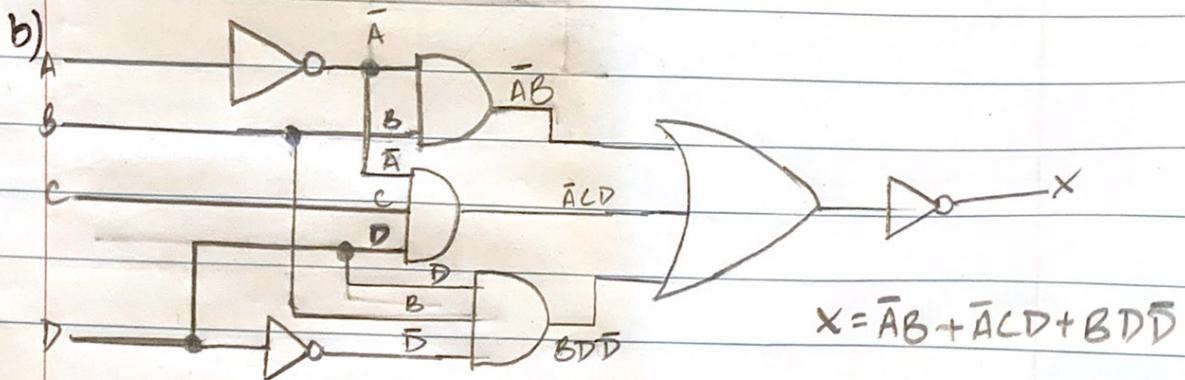

$$\begin{aligned}
 X &= (\bar{A}B + \bar{A}CD + BD\bar{D}) \\
 &= (\bar{A}B)(\bar{A}CD)(BD\bar{D}) \\
 &= (A+\bar{B})(A+\bar{C}+\bar{D})(\bar{B}+\bar{D}+D) \\
 &= (A+\bar{B})(A+\bar{C}+\bar{D})(\bar{B}+1) \\
 &= (A+\bar{B})(A+\bar{C}+\bar{D})
 \end{aligned}$$

* $\bar{D} + D = 1$

* $1 + \bar{B} = 1$

$$X = A + \bar{B}(\bar{C} + \bar{D})$$