

Almed El Ghaour

Electronics II: Test 3

$$\begin{aligned} \textcircled{2} \quad R_L &= R_o \parallel R_D \\ &= 40000 \parallel 8000 \\ &= 6.7 \text{ K}\Omega \end{aligned}$$

$$\Rightarrow A = -g_m R_L$$
$$= -(5000 \times 10^{-6}) (6.7 \times 10^3)$$

$$\boxed{A = -33.5}$$

Let determine the factor  $\beta$

$$\beta = \frac{-R_2}{R_1 + R_2} = \frac{-20000}{20000 + 80000} = -0.2$$

$$A_f = \frac{A}{1 + \beta A} = \frac{-33.5}{1 + (-0.2)(-33.5)}$$

$$\boxed{A_f = -4.4}$$

① we know that  $A_f = \frac{A}{1 + \beta A}$

if  $A = -1000$

$$A_{f1} = \frac{-1000}{1 + (-1/15)(-1000)} = -14.78$$

Let determine  $A_f$  at  $A = -1000$  (1.1)

$$A_{f2} = \frac{-1000 \cdot (1.1)}{1 + (-1/15)(-1000 \cdot (1.1))} = -14.8$$

$$\Delta A_f = \left| \frac{A_{f1} - A_{f2}}{A_{f1}} \right| \times 100\% = \left| \frac{-14.78 + 14.8}{-14.78} \right| \times 100\%$$

$$= \left| \frac{+0.2}{-14.78} \right| \times 100\% = 0.0135 \times 100\% = 1.35\%$$

$$\Delta A_f = 0.18\%$$

$$(3) V_{pc} = \frac{2.4 I_{dc}}{r_C} = \frac{2.4(200)}{(0.08)(500)} = 12V$$

$$V_{DC} = 12V$$

$$V_m = V_{dc} + \frac{4.17 I_{dc}}{C} = 12 + \frac{4.17(200)}{500} = 13.7V$$

$$V_m = 13.7V$$

$$(4) V_o = V_Z + V_{BE}$$

$$= 10 + 0.7 = 10.7V$$

$$(5) C_T(V_R) = \frac{C(0)}{\left(1 + \left|\frac{V_R}{V_T}\right|\right)^n}$$

Since the junction is diffused  $n = \frac{1}{3}$

$$C_T(V_R) = \frac{80 \times 10^{-12}}{\left(1 + \left|\frac{4.2}{0.7}\right|\right)^{1/3}}$$

therefor  $C_T = 41.82 \text{ pF}$

$$(6) \quad C_t = 93 \text{ pF}$$

$$C_t = 5.6 \text{ pF}$$

$$\text{the Ratio} = \frac{93 \times 10^{-13}}{5.6 \times 10^{-12}} = \boxed{16.61}$$

$C_t = 80 \text{ pF}$ , At a reverse potential of  $1.25 \text{ V}$

$$C_t = 6 \text{ pF}$$

$$\text{the Ratio} = \frac{80 \times 10^{-12}}{6 \times 10^{-12}} = 13.33 \text{ "Decreased"}$$