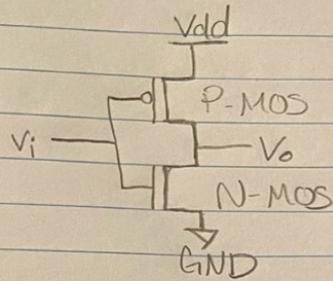


1) Lab 1 VLSI Tamara Boyd  
Transistor level of inverter



2) Stick Diagram of the Inverter

